

## **TRANSISTOR CE CHARACTERISTICS**

**AIM:** To draw the input and output characteristics of transistor connected in CE configuration

### **APPARATUS:**

Transistor (SL100 or BC107)

R.P.S (0-30V)                      2Nos

Voltmeters (0-20V)              2Nos

Ammeters (0-200mA)

Resistors    100Kohm, 100ohm

Bread board and connecting wires

### **THEORY:**

A transistor is a three terminal device. The terminals are emitter, base, collector. In common emitter configuration, input voltage is applied between base and emitter terminals and out put is taken across the collector and emitter terminals.

Therefore the emitter terminal is common to both input and output.


The input characteristics resemble that of a forward biased diode curve. This is expected since the Base-Emitter junction of the transistor is forward biased. As compared to CB arrangement  $I_B$  increases less rapidly with  $V_{BE}$ . Therefore input resistance of CE circuit is higher than that of CB circuit.

The output characteristics are drawn between  $I_C$  and  $V_{CE}$  at constant  $I_B$ . the collector current varies with  $V_{CE}$  upto few volts only. After this the collector current becomes almost constant, and independent of  $V_{CE}$ . The value of  $V_{CE}$  up to which the collector current changes with  $V_{CE}$  is known as Knee voltage. The transistor always operated in the region above Knee voltage,  $I_C$  is always constant and is approximately equal to  $I_B$ .

The current amplification factor of CE configuration is given by

$$B = \Delta I_C / \Delta I_B$$

**CIRCUIT DIAGRAM:**

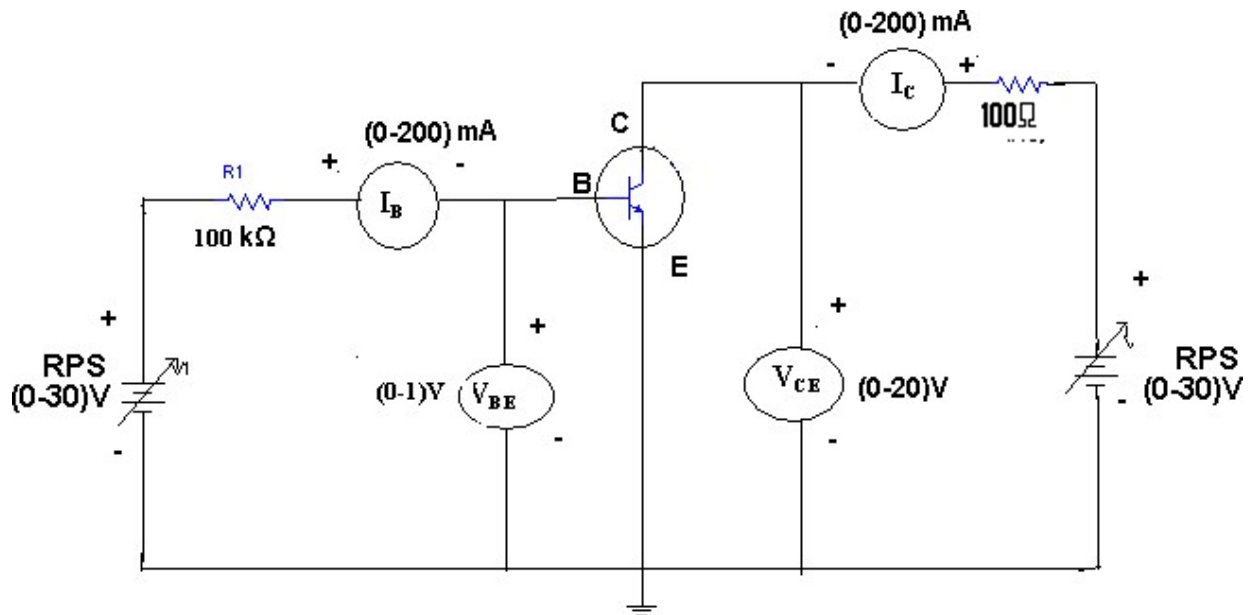

**PROCEDURE:**

**INPUT CHARACTERISTICS:**

1. Connect the circuit as per the circuit diagram.
2. For plotting the input characteristics the output voltage  $V_{CE}$  is kept constant at 1V and for different values of  $V_{BE}$ . Note down the values of  $I_C$ .
3. Repeat the above step by keeping  $V_{CE}$  at 2V and 4V.
4. Tabulate all the readings.
5. plot the graph between  $V_{BE}$  and  $I_B$  for constant  $V_{CE}$

**OUTPUT CHARACTERISTICS:**

1. Connect the circuit as per the circuit diagram
2. for plotting the output characteristics the input current  $I_B$  is kept constant at 10 $\mu$ A and for different values of  $V_{CE}$  note down the values of  $I_C$
3. repeat the above step by keeping  $I_B$  at 75  $\mu$ A 100  $\mu$ A

## Electronics Laboratory

4. tabulate the all the readings
5. plot the graph between  $V_{CE}$  and  $I_C$  for constant  $I_B$

### OBSERVATIONS:

#### INPUT CHARACTERISTICS:


S.NO	$V_{CE} = 1V$		$V_{CE} = 2V$		$V_{CE} = 4V$	
	$V_{BE}(V)$	$I_B(\mu A)$	$V_{BE}(V)$	$I_B(\mu A)$	$V_{BE}(V)$	$I_B(\mu A)$

#### OUT PUT CHAREACTARISTICS:


S.NO	$I_B = 50 \mu A$		$I_B = 75 \mu A$		$I_B = 100 \mu A$	
	$V_{CE}(V)$	$I_C(mA)$	$V_{CE}(V)$	$I_C(mA)$	$V_{CE}(V)$	$I_C(mA)$

**MODEL GRAPHS:**

**INPUT CHARACTERISTICS:**

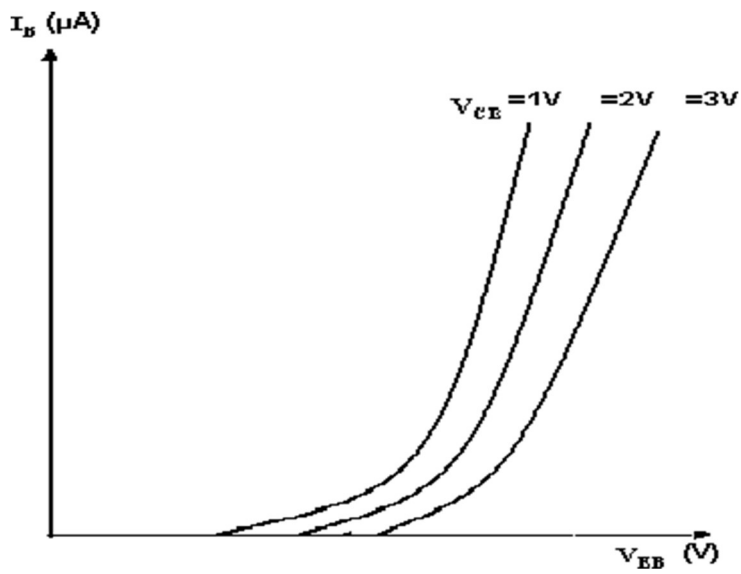

**OUTPUT CHARACTERISTICS:**

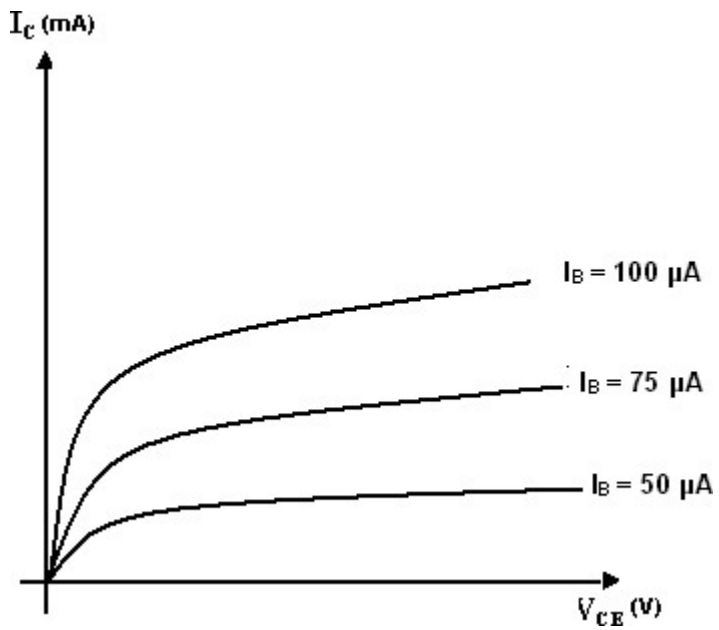

**PRECAUTIONS:**

1. The supply voltage should not exceed the rating of the transistor
2. Meters should be connected properly according to their polarities

**VIVA QUESTIONS:**

1. What is the range of  $\beta$  for the transistor?
  2. What are the input and output impedances of CE configuration?
  3. Identify various regions in the output characteristics?
  4. what is the relation between  $\alpha$  and  $\beta$
  5. Define current gain in CE configuration?
  6. Why CE configuration is preferred for amplification?
  7. What is the phase relation between input and output?
  8. Draw diagram of CE configuration for PNP transistor?
  9. What is the power gain of CE configuration?
  10. What are the applications of CE configuration?
-